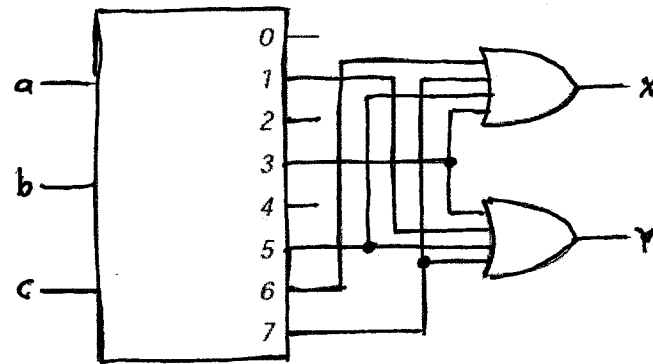


Chapter 5; Problem 7: consider the following circuit with an active high output decoder. Draw a truth table for x and y in terms of a, b and c .



Logic Expression for x and y

$$x(a, b, c) = \sum m(3, 5, 6, 7)$$



$$y(a, b, c) = \sum m(1, 3, 5, 7)$$

Truth Table \Rightarrow

a	b	c	x	y
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1

Chapter 5 problem 8: We wish to design a decoder, with three inputs, x, y, z and eight active high outputs, labeled $0, 1, 2, 3, 4, 5, 6, 7$. There is no enable input required. The only building block is a two-input, four output decoder (with an active high enable).

EN	A	B	0	1	2	3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

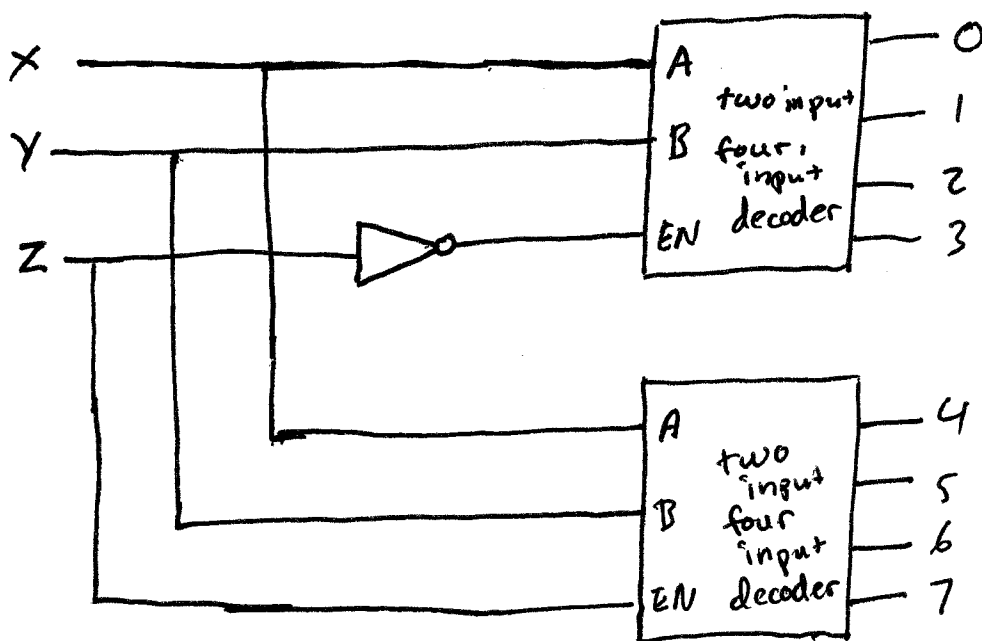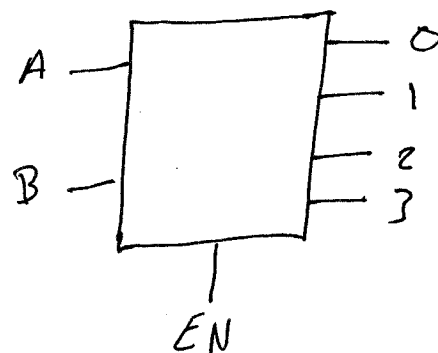


Chapter 5 problem 9: We want to implement a full adder: we'll call the inputs a, b and c and the outputs S and $Count$. As always, the adder is described by the following equations.


$$S(a, b, c) = \sum m(1, 2, 4, 7)$$

$$Count(a, b, c) = \sum m(3, 5, 6, 7)$$

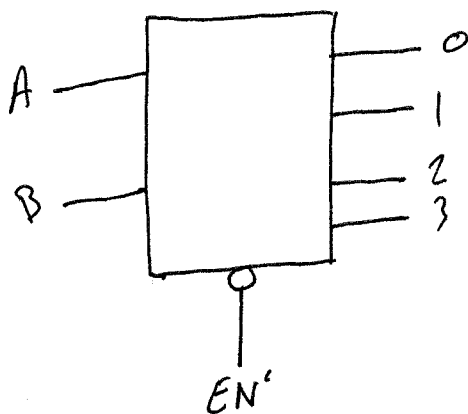To implement this, all we have available are two decoders and two OR gates. Inputs a and b are available both uncomplemented and complemented; c is available only uncomplemented. Show a block diagram for this system. Be sure to label all of the inputs to the decoders.




EN'	A	B	0	1	2	3
1	x	x	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1

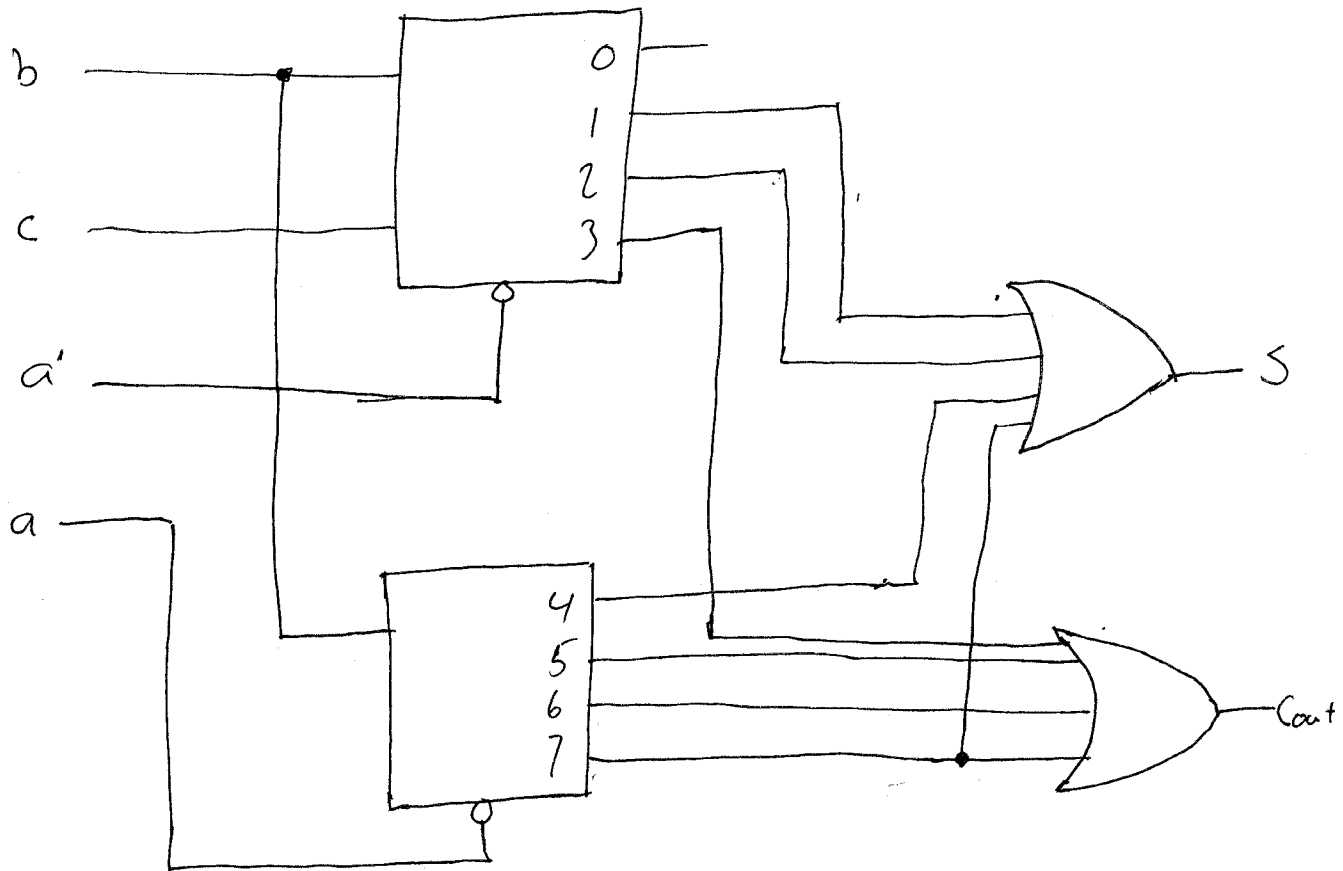


Chapter 5 problem 12: Implement the function

$$F(x, y, z) = \sum m(0, 1, 3, 4, 7)$$

use 2:1 multiplexers

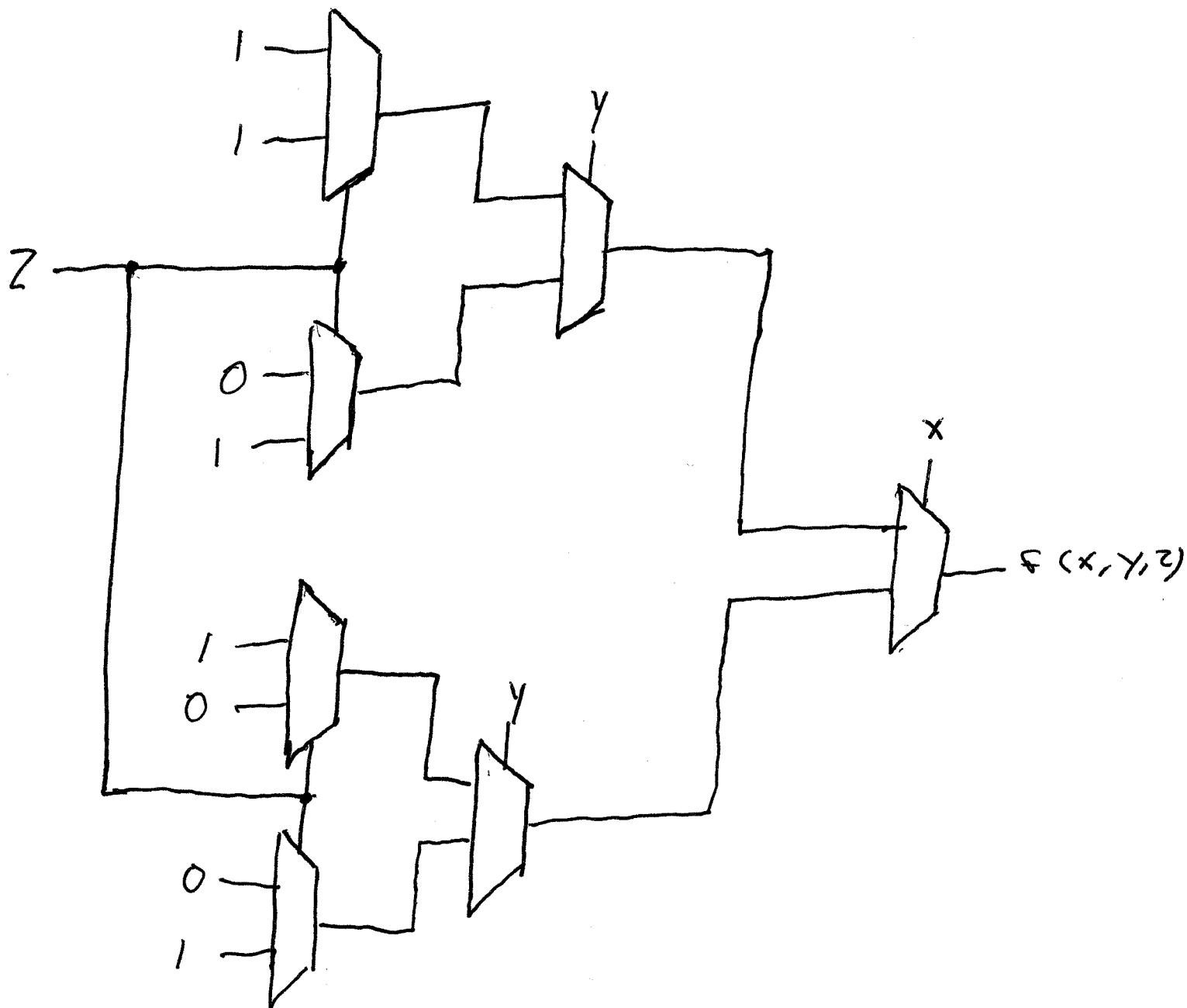

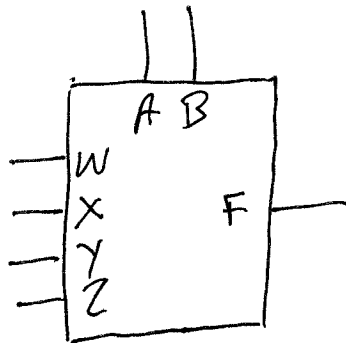Chapter 5, problem 12: The following circuit includes a multiplexer with select inputs A and B and data inputs W, X, Y and Z. Write an algebraic equation for F.



Truth Table =

A	B	F
0	0	W
0	1	X
1	0	Y
1	1	Z

Algebraic Equation:

$$F = ABW + ABX + ABY + ABZ$$


Chapter 5, problem 15: For the following sets of functions,
design a system

i: Using a ROM

$$a) F(A, B, C) = \sum m(3, 4, 5, 7)$$

$$G(A, B, C) = \sum m(1, 3, 5, 6, 7)$$

$$H(A, B, C) = \sum m(1, 4, 5)$$

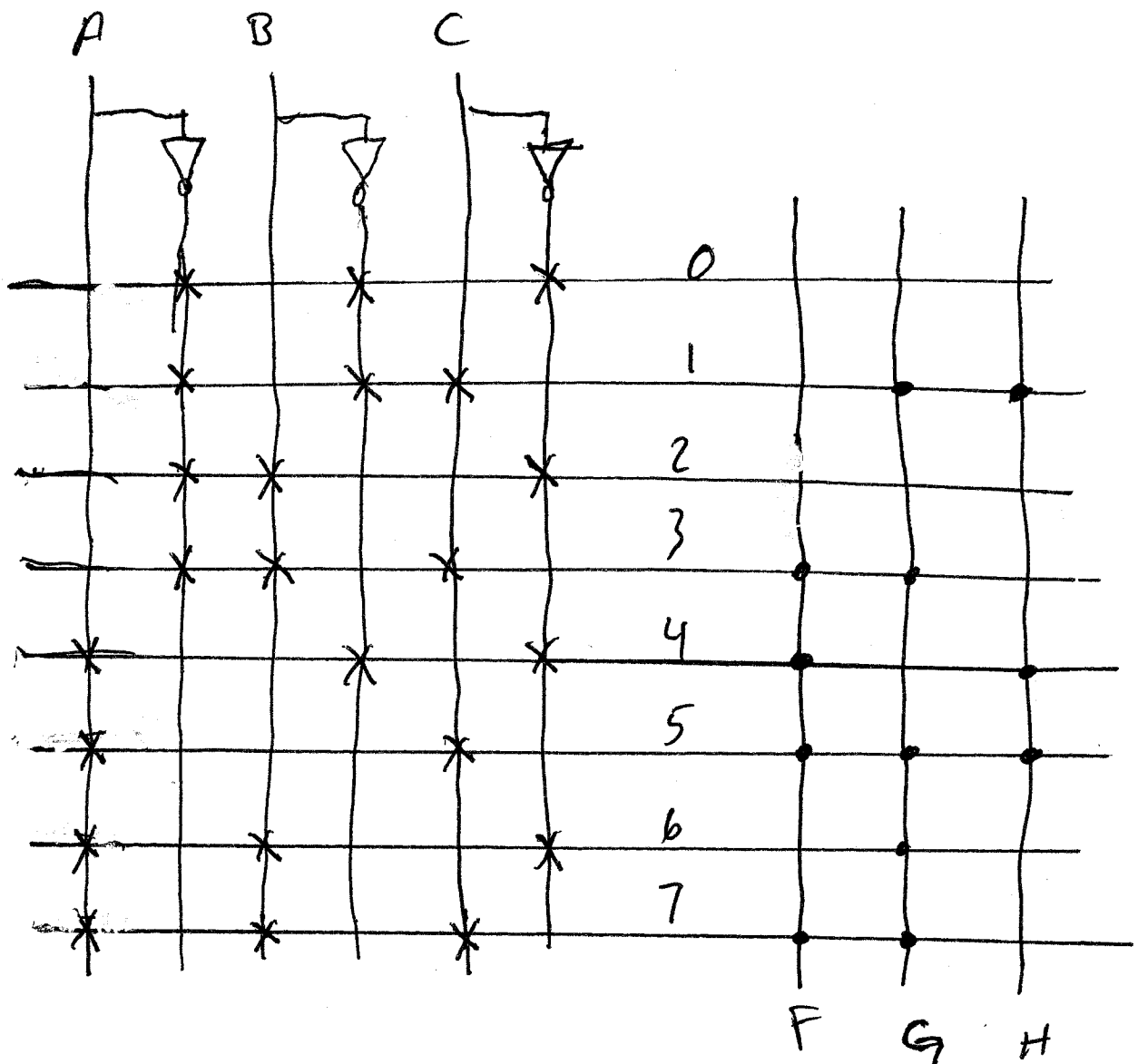

Chapter 5, Problem 16: We have found a minimum sum of products expression for each of the two functions, F and G, minimizing them individually.

$$F = w'x'y + xy'z + w'z$$

$$G = wy'z + x'y'$$

(a) Implement them with a BOM

$$F = w'x'y + xy'z + w'z$$

$$= w'x'y'(z+z') + xy'z(w+w') + w'z(x+x')(y+y')$$

$$= w'x'y'z + w'x'y'z' + wxy'z + w'xy'z + xw'z(y+y') + x'w'z(y+y')$$

$$F = w'x'y'z + w'x'y'z' + wxy'z + w'xy'z + w'xyz + w'x'y'z$$

$$G = wy'z + x'y'$$

$$= wy'z(x+x') + x'y'(w+w')(z+z')$$

$$= xwy'z + x'wy'z + wx'y'(z+z') + w'x'y'(z+z')$$

$$= wx'y'z + wx'y'z + wx'y'z + wx'y'z + w'x'y'z + w'x'y'z$$


$$G = wx'y'z + wx'y'z + wx'y'z + wx'y'z + w'x'y'z + w'x'y'z$$

F

$y_2 \backslash wx$	00	01	11	10
00	1			
01	1	1	1	
11	1	1		
10				

G

$y_2 \backslash wx$	00	01	11	10
00	1			1
01	1		1	1
11				
10				1

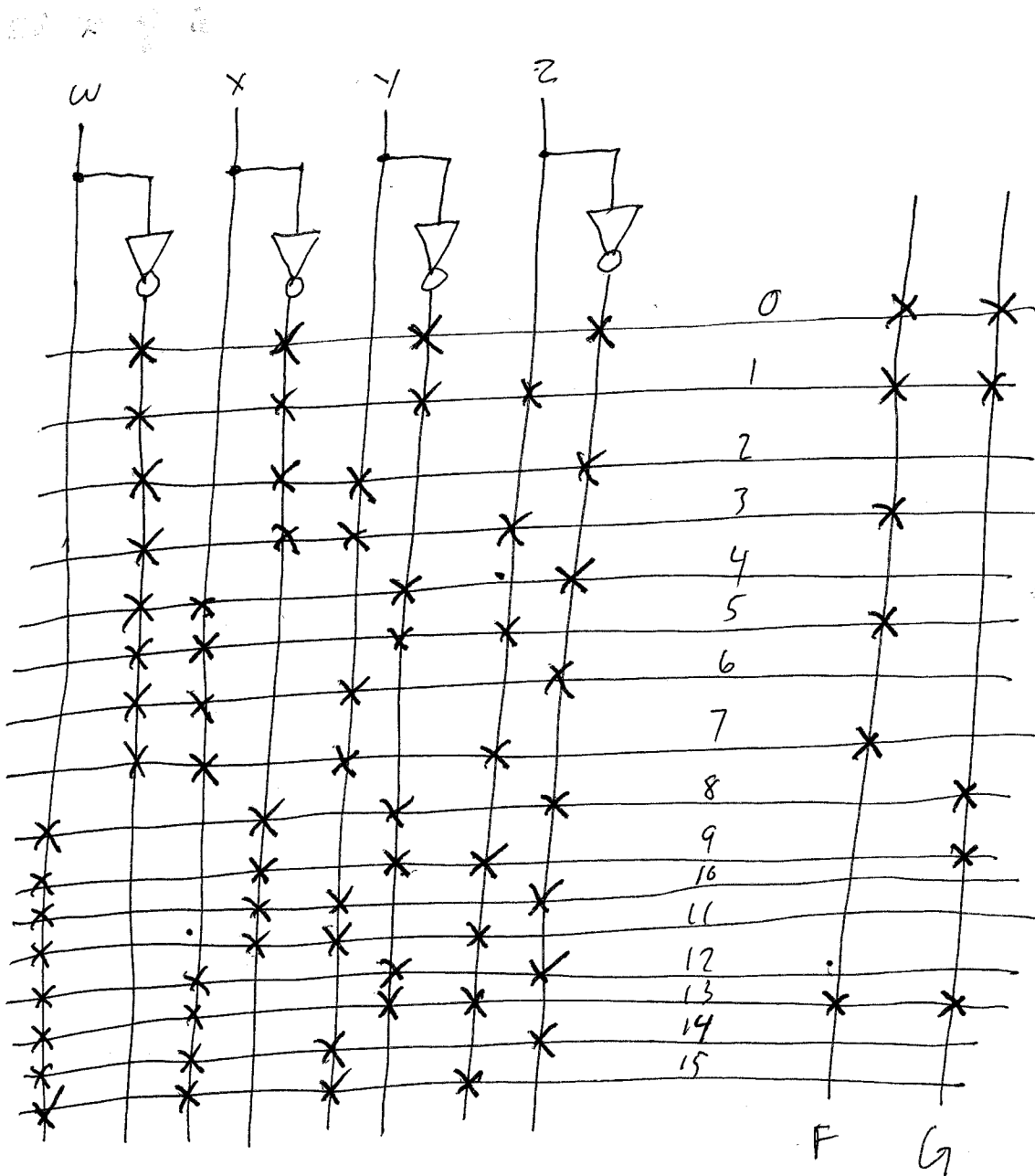

(C) For the same function, we have available as many of the decoders as described in the assignment as are needed. plus 2 eight-input OR gates. show a block diagram for this implementation. All inputs are available both uncomplemented and complemented.

